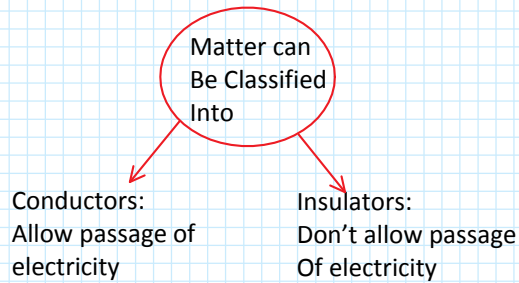


# Physics DC-Voltage Summary

Tuesday, January 3, 2023 11:28 AM



1. **Voltage (V):** Measures the difference in potential between 2 points

$$V_{PN} = -V_{NP}$$

- If  $V_{\text{drycell}} = \text{rated voltage}$  → Lamp functions normally
- If  $V_{\text{drycell}} > \text{rated voltage}$  → Lamp will burn out
- If  $V_{\text{drycell}} < \text{rated voltage}$  → Lamp will glow weakly

2. **Electric current:** Due to the flow of charges in a unit of time

3. **Voltmeter:**

- ✓ Used to measure voltage
- ✓ Connected in parallel
- ✓ Com terminal must be connected to the -Ve pole →

★ **Remark!!!!!!!:** If the connection of the voltmeter is reversed

↓  
A negative reading for the voltage measured will be given

4. **Ammeter:**

- ✓ Used to measure current
- ✓ Connected in series
- ✓ Com terminal must be connected to the -Ve pole

★  $V_{AB} = V_{\text{closed switch}} = 0V$

★  $V_{\text{open switch}} = V_{\text{dry cell}}$

★ **The voltage across a connecting wire = 0V**

5. **Parallel connection**

- Law of addition of current ( $I_{\text{main}} = I_{L_1} + I_{L_2}$ )
- Law of uniqueness of voltage ( $V_{L_1} = V_{L_2}$ )

6. **Series connection**

- Law of uniqueness of current ( $I_{\text{main}} = I_{L_1} + I_{L_2}$ )
- Law of addition of voltage:  
 $V_{PN} = V_{AB} + V_{BC}$   
OR



$$V_{PN} = V_{L_1} + V_{L_2}$$

★ **Remark!!!!!!!:** If the lamps are identical →  $V_{PN}$  will be divided equally on both lamps


$$V_{L_1} = V_{L_2} = \frac{V_{PN}}{2}$$

7. **Oscilloscope** : Device used to measure and display the electric voltage (**Signal**)

→ **Connection of the Oscilloscope:**

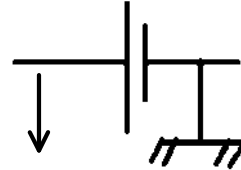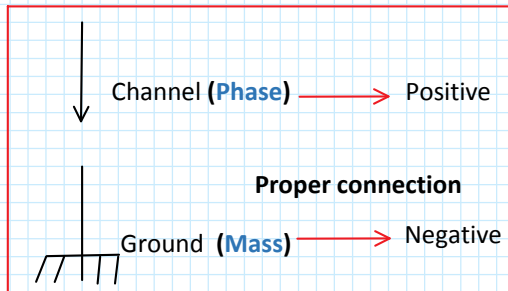
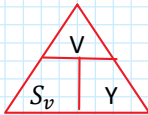
$$V_{dry\ cell} = V_{PN} = V_{phase} \rightarrow V_{ground}$$




$$V_{dry\ cell} = V_{PN} = S_v \times Y$$

Number of divisions on the y-axis (**div**)

Scale on the Vertical (**Vertical sensitivity**) (**V/div**)

Measured Voltage (**V**)

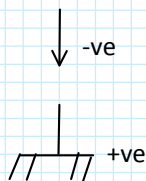★ **Remark!!!!!!!:** If the connection of the oscilloscope are reversed



Luminous line will be displaced downward